

CSD1100

Memory Circuit

Vadim Surov

Outline


- Combinatorial and Sequential logic
- RS-Flip-Flop
- D-Flip-Flop
- Memory Address And Units
- Layout
- Address decoder
- Storage Elements
- How to store numbers and characters
- Big- and Little-Endian Formats
- Self-test questions

Sequential logic

- **Combinatorial logic** circuits output depends only on the inputs. Ex: half and full adders.
- **Sequential logic** is a type of logic circuit whose output depends not only on the present value of its input signals but on the sequence of past inputs
- Sequential logic has state (memory) while combinational logic does not.


Reset, Set Flip-Flop (RS-Flip-Flop)

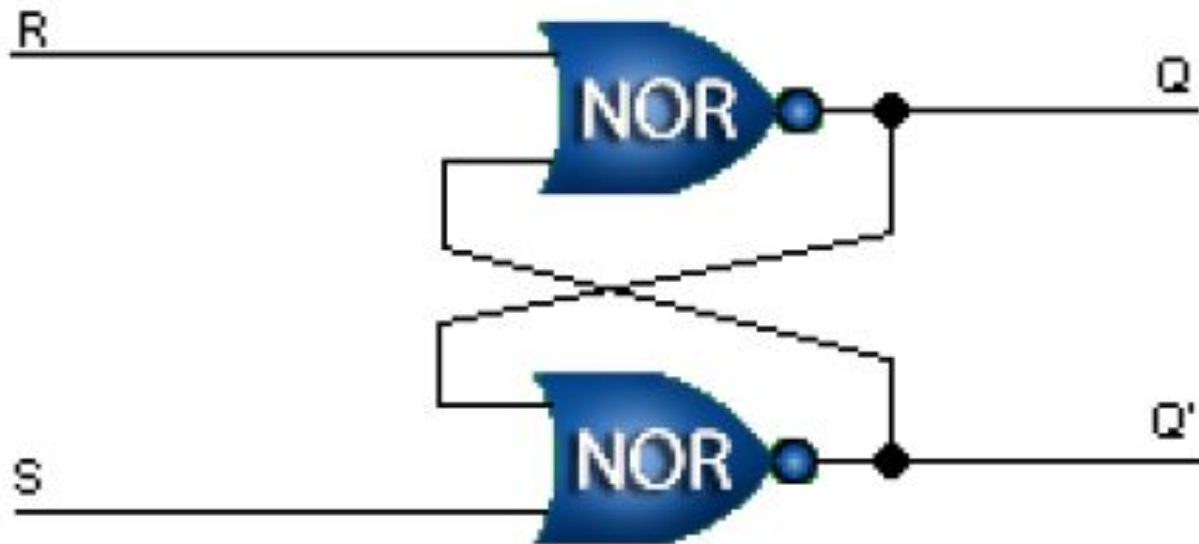- RS-flip-flop is the simplest possible memory element.
- The RS-flip-flop is composed of two NOR gates. (Can also be constructed from NAND gates)




- The output Q is the opposite of Q' .

RS-Flip-Flop Truth Table

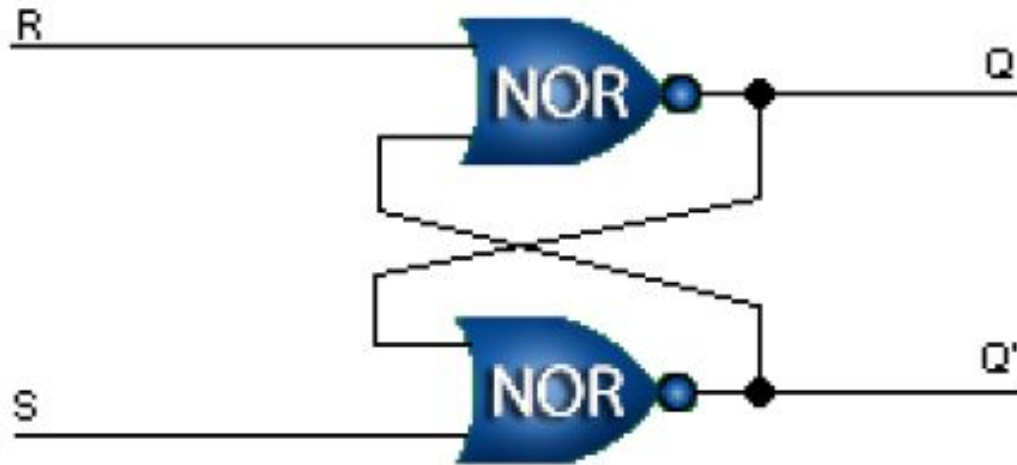

<u>R</u>	<u>S</u>	<u>Q</u>	<u>Q'</u>	<u>Description</u>
0	0	Q	Q'	Hold state
0	1	1	0	Set
1	0	0	1	Reset
1	1	?	?	Not Allowed


RS-Flip-Flop Truth Table

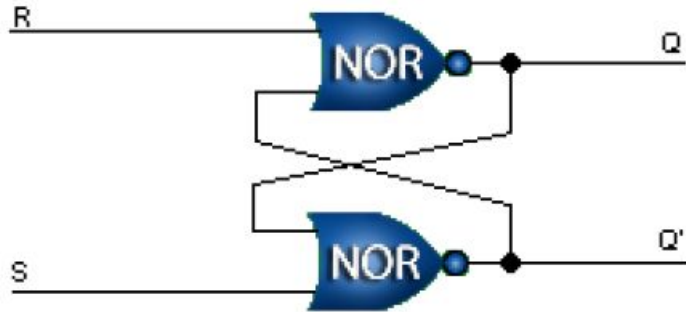

<u>R</u>	<u>S</u>	<u>Q</u>	<u>Q'</u>	<u>Description</u>
0	0	Q	Q'	Hold state
0	1	1	0	Set
1	0	0	1	Reset
1	1	?	?	Not Allowed

- When $S=1$ and $R=0$.
 - The output at the bottom NOR gate is equal to zero ($Q' = 0$).
 - Hence, both inputs to the top NOR gate are equal to zero, thus $Q = 1$.
 - Implies that the input combinations $S=1$ and $R=0$ leads to the Flip-flop being set to $Q=1$.


RS-Flip-Flop Truth Table

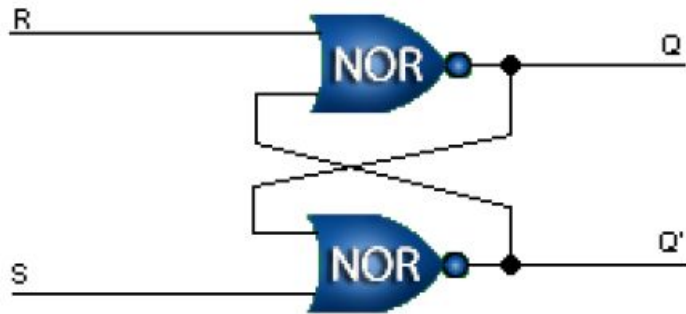

<u>R</u>	<u>S</u>	<u>Q</u>	<u>Q'</u>	<u>Description</u>
0	0	Q	Q'	Hold state
0	1	1	0	Set
1	0	0	1	Reset
1	1	?	?	Not Allowed

- When $S=0$ and $R=1$.
 - The output becomes $Q=0$ and $Q'=1$.
 - We say that the flip-flop is reset.


RS-Flip-Flop Truth Table

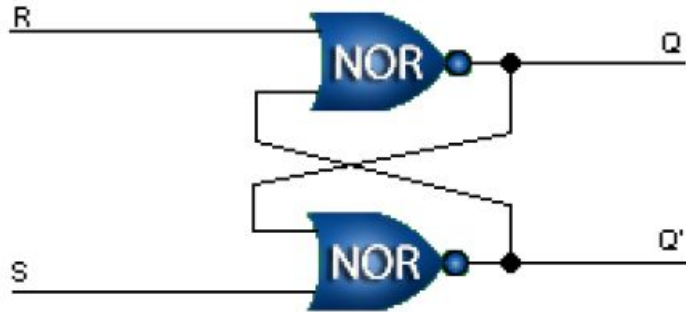

<u>R</u>	<u>S</u>	<u>Q</u>	<u>Q'</u>	<u>Description</u>
0	0	Q	Q'	Hold state
0	1	1	0	Set
1	0	0	1	Reset
1	1	?	?	Not Allowed

- When $S=0$, $R=0$, $Q=0$ and $Q'=1$.
 - The output at the top NOR gate remains at $Q=0$.
 - The output at the bottom NOR gate stays at $Q'=1$.


RS-Flip-Flop Truth Table

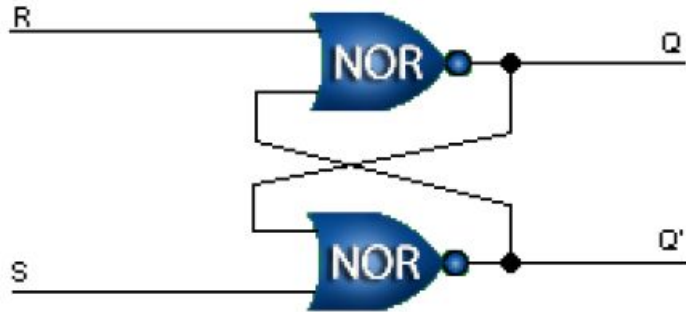

R	S	Q	Q'	Description
0	0	Q	Q'	Hold state
0	1	1	0	Set
1	0	0	1	Reset
1	1	?	?	Not Allowed

- When $S=0$, $R=0$, $Q=1$ and $Q'=0$.
 - The output at the top NOR gate remains at $Q=1$.
 - The output at the bottom NOR gate stays at $Q'=0$.
- Therefore, when $S=0$ and $R=0$, the flip-flop remains in its state.


RS-Flip-Flop Truth Table

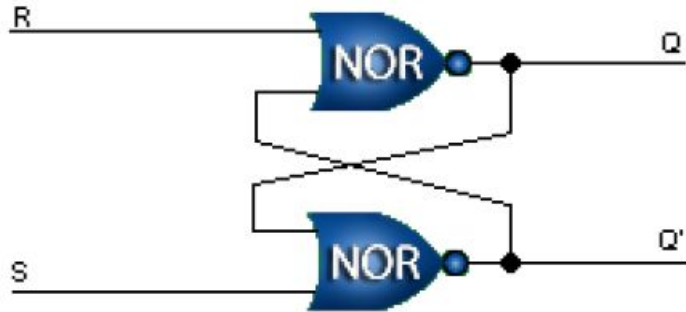

<u>R</u>	<u>S</u>	<u>Q</u>	<u>Q'</u>	<u>Description</u>
0	0	Q	Q'	Hold state
0	1	1	0	Set
1	0	0	1	Reset
1	1	?	?	Not Allowed


- S=1 and R=1 is not allowed. Therefore, it should be avoided.

Data-Flip-Flop (D-Flip-Flop)

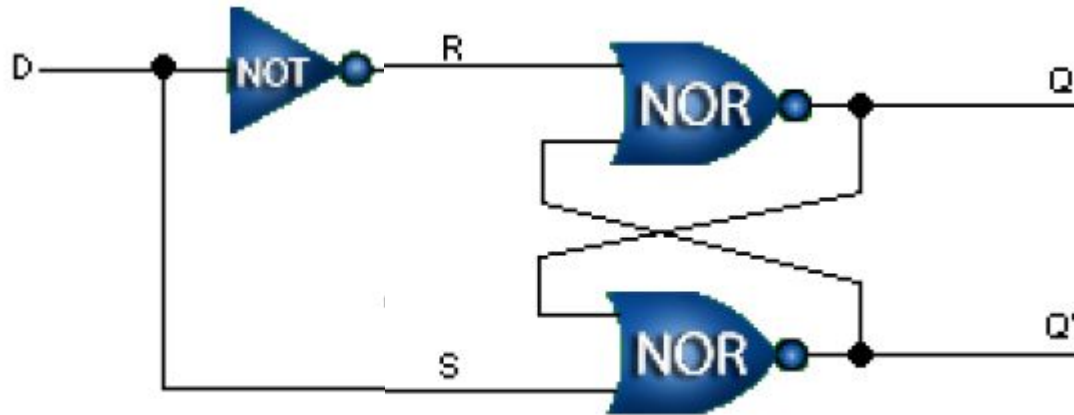


- The D-flip-flop has a single data input.
 - The data input is connected to the S input of an RS-flip-flop.
 - The inverse of the D is connected to the R input.
- The $S=1$ and $R=1$ combination will never occur.

Data-Flip-Flop (D-Flip-Flop)

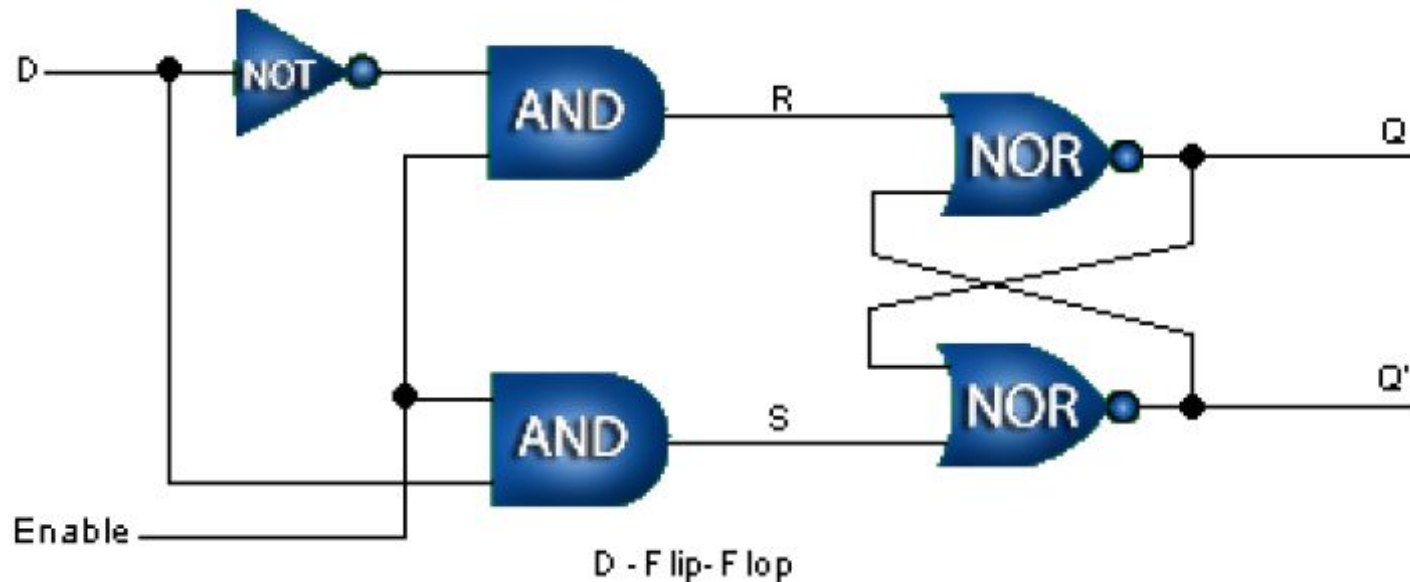


- To allow a flip-flop to be in a holding state, an additional Enable input is required.
- The Enable input is AND-ed with the D input.
- When Enable=0, then R=0 and S=0. Therefore, the flip-flop state is held.

Data-Flip-Flop (D-Flip-Flop)

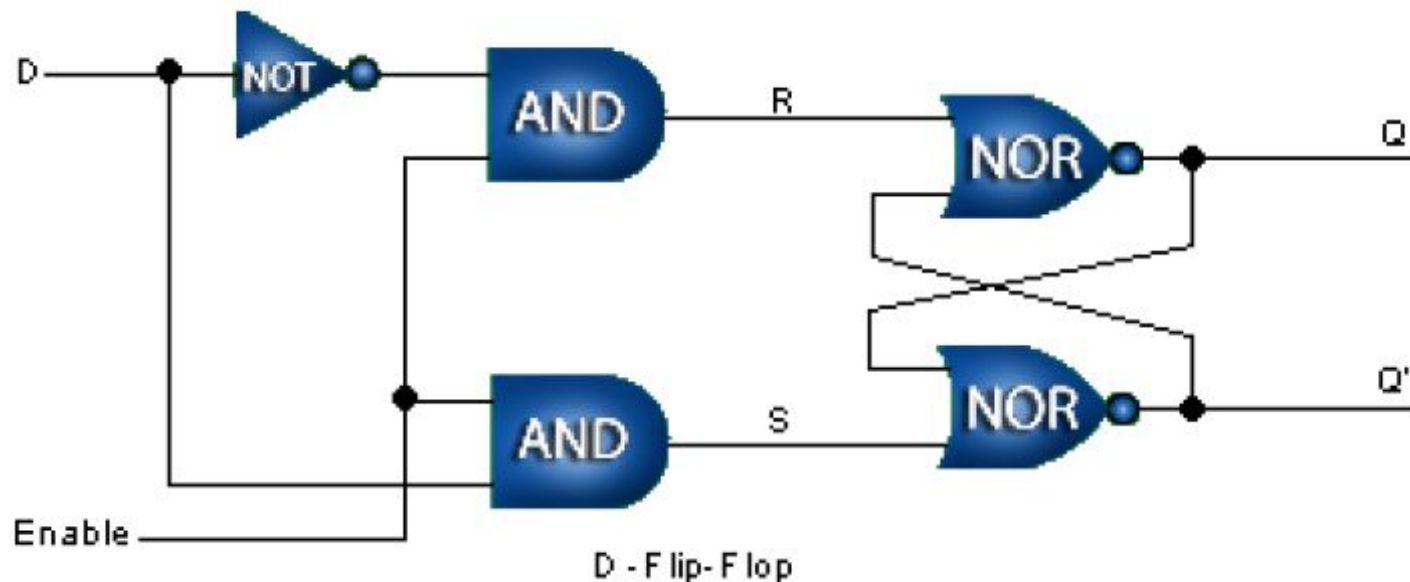

- When Enable=1, $S=D$ and R is the inverse of D , then the value of D determines the value of the output Q when Enable=1.
- When Enable returns to 0, the most recent input D is remembered.

D-Flip-Flop Truth Table

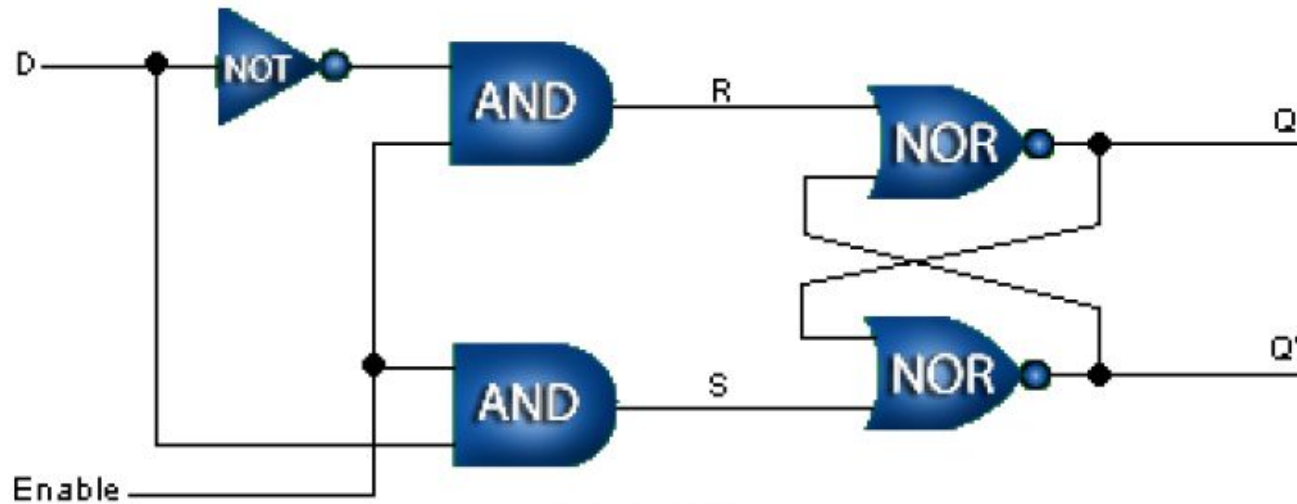

<u>E</u>	<u>D</u>	<u>Q</u>	<u>Q'</u>	<u>Description</u>
0	0	Q	Q'	Hold state
0	1	Q	Q'	Hold state
1	0	0	1	Reset
1	1	1	0	Set


Memory Address And Units

- RAM is made up of **storage elements**, 8-bits each.
- Storage elements could be similar to the D-flip-flop.
- Every storage element has a unique address as a number to read from or write to a particular storage element.

- **Byte** = 8 bits the smallest addressable unit for a CPU.
- **Word** - the natural size with which a processor is handling data, for example, using registers. The most common word sizes encountered today are 32 and 64 bits.
- 1024 bytes = 1 **Kilobyte** (KB). 1024 KB = 1 **Megabyte** (MB). 1024 MB = 1 **Gigabyte** (GB).


Layout

- Storage elements are arranged on a square grid of columns and rows.
- Ex: 1 Megabit = 128 Kilobyte of RAM consists of 1024 rows and 1024 columns of storage elements.
- Each individual storage element can be identified through its coordinates. In other words, **individual storage elements can be identified by their row and column.**
- To address a particular storage element, the address information must be translated into row and column specification.

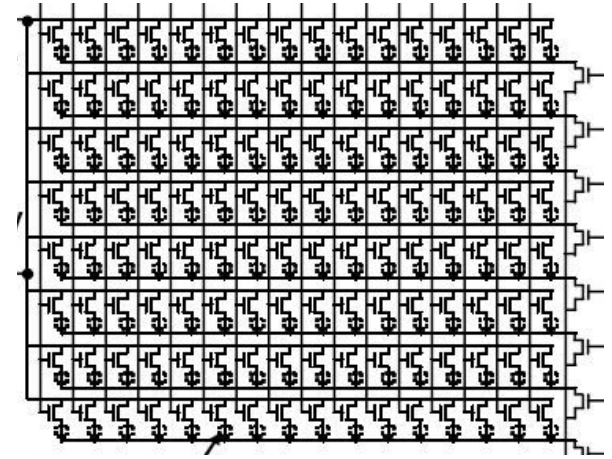

Layout

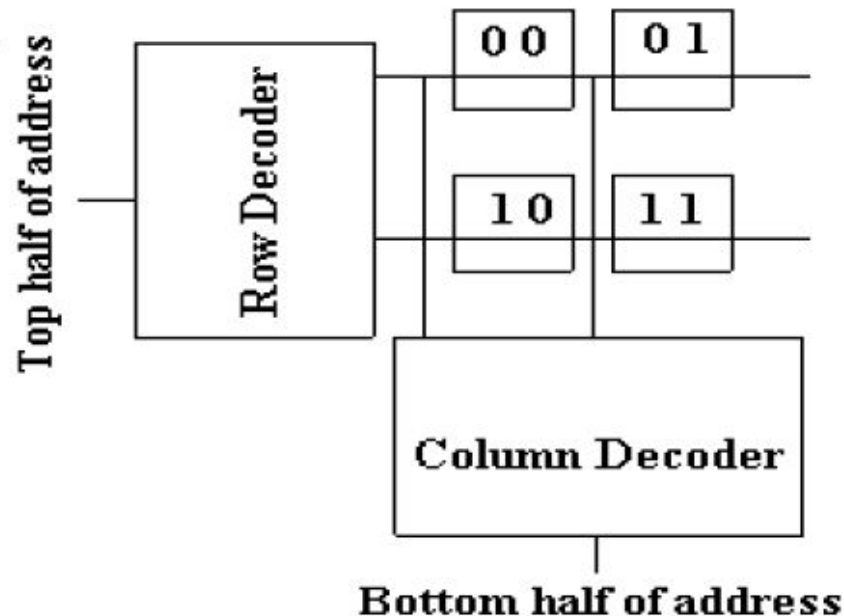- The address information is divided into two parts.
 - The top half is used to select the row.
 - The bottom half is used to select the column.
- A 4-bit RAM figure will look like this:




Address decoder


- The address decoder has a binary number with N bits as its input. It has 2^N outputs.
- At any time, only one output line is '1' and all the others are '0s'.
- The line that is '1' specifies the desired column or row.

Address decoder

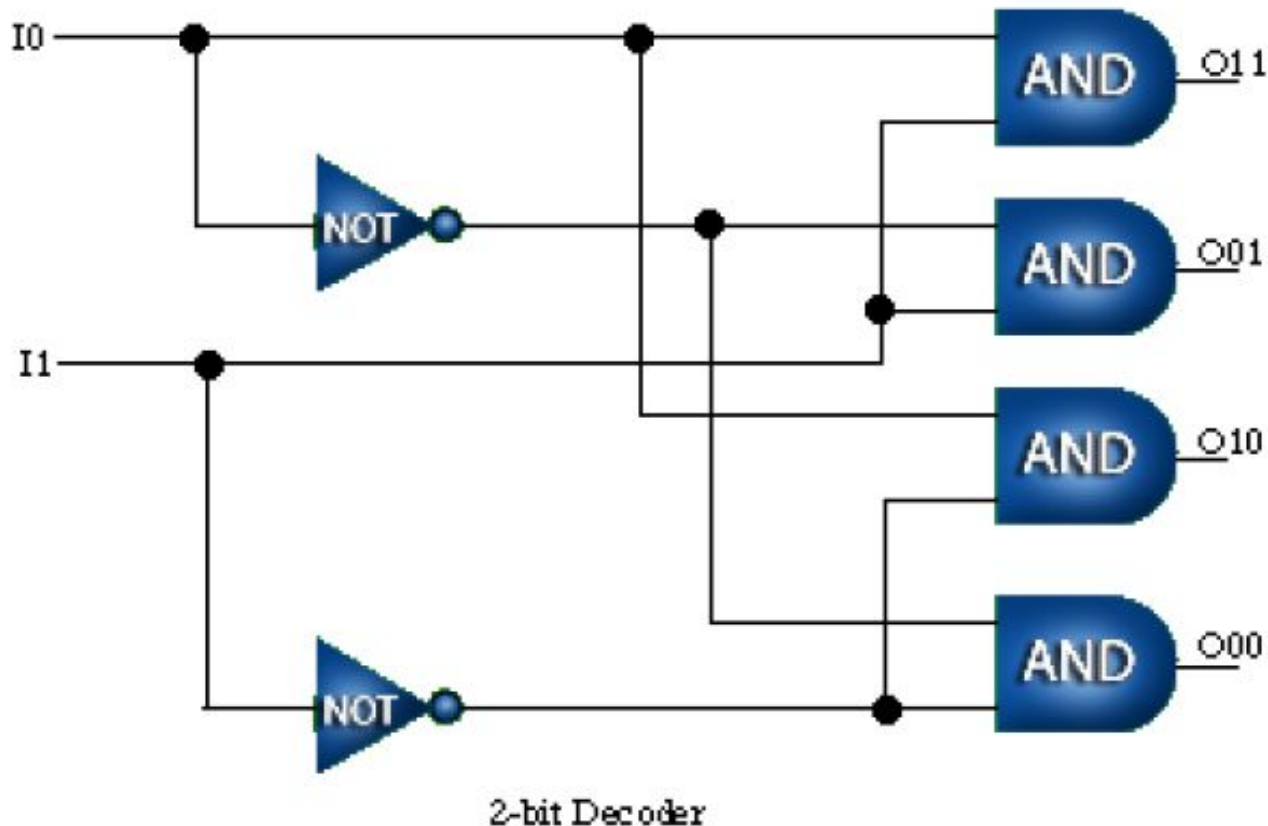- Example of a decoder with 2 inputs and 4 ($=2^2$) outputs:




Address decoder. Truth Table

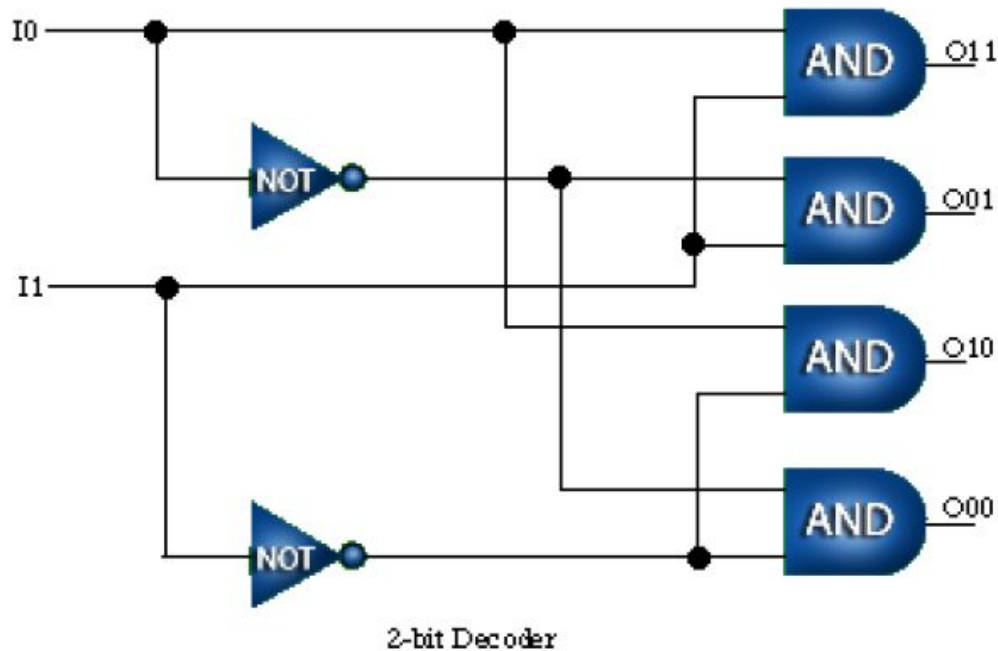

Input		Output			
I0	I1	O11	O10	O01	O00
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0


Storage Elements

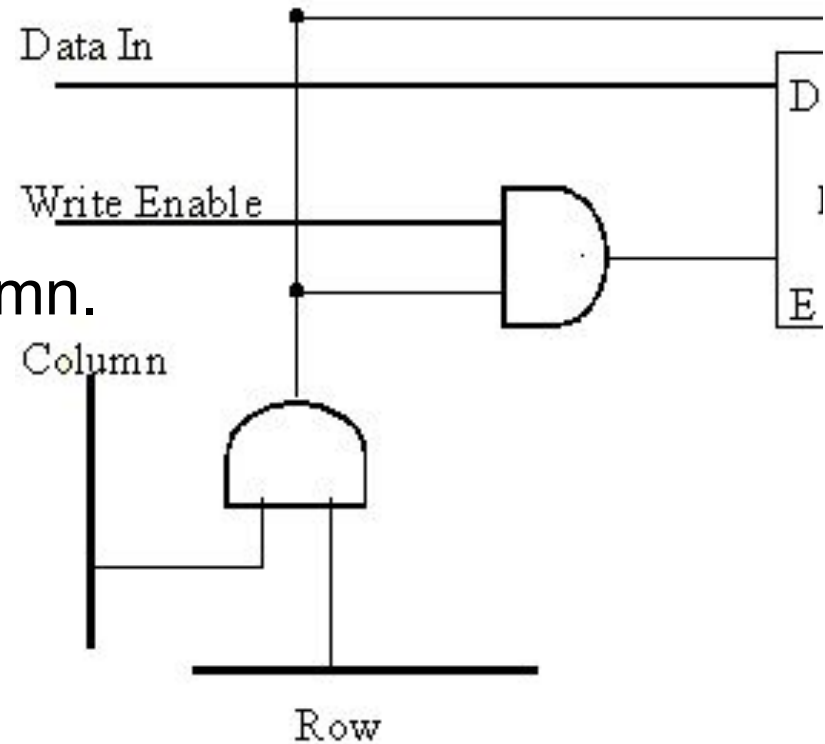- Each storage element is connected to one row and column.
- Since for every address, only one row and one column selector line will be '1', exactly one storage element can be selected.
- The storage element is selected by AND-ing its row and its column selector line.
- If a D-flip-flop is used as a storage element and connect its Enable input to the output of the AND gate mentioned above.




Storage Elements

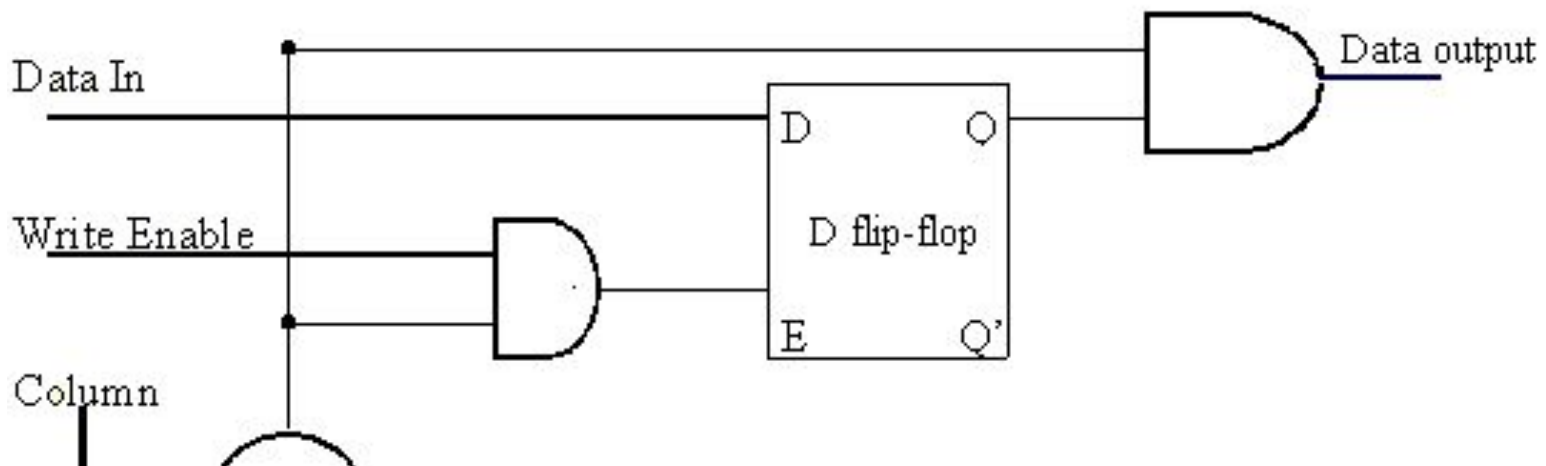- The D-input is connected to the data input line that is common to all storage elements.
- The output of the flip-flop is AND-ed with the output of the first AND gate and then connected to a data output line that is common to all storage elements.
- Only the selected storage element contributes to the common output line.




Storage Elements

- The read process should Leave the value of the gate unchanged.
- To prevent data destruction during a read operation a 'Write Enable' signal is introduced.
- The signal is '1' only when new data is to be stored.
- It is AND-ed with the output of the first AND gate and then applied to the flip-flop's enable input.
- During read operations, the 'Write Enable' is '0', the flip-flop is disabled and does not change its state.

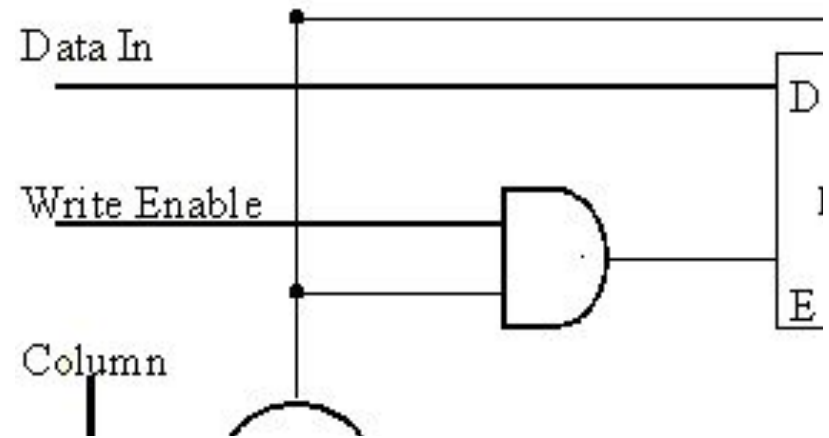

Storage Elements

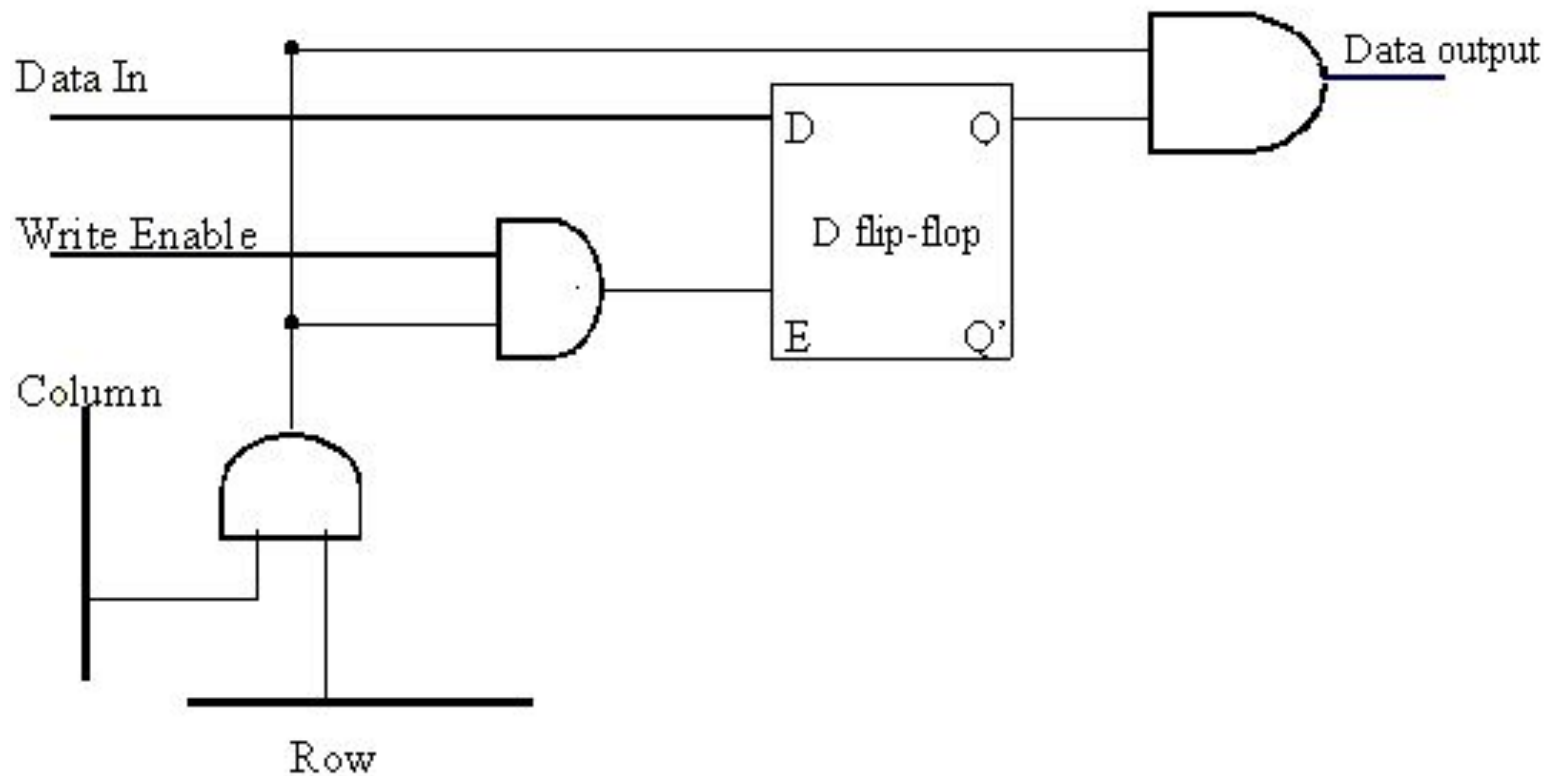

How to store numbers in memory

- A computer machine's memory is an array of consecutively numbered or addressed memory cells holding a bit value.
- Every byte in a machine memory has a unique number or address.

How to store numbers in memory. Example 1

- If we have a memory size of 8 bytes, memory address 0 will point to the first byte, memory address 1 will point to the second byte and memory address 7 will point to the last byte, byte number 8. This is what the empty memory will look like:

Address	Content	
0	00000000	(8 bits)
1	00000000	(8 bits)
2	00000000	(8 bits)
3	00000000	(8 bits)
4	00000000	(8 bits)
5	00000000	(8 bits)
6	00000000	(8 bits)
7	00000000	(8 bits)

How to store numbers in memory. Example 2

- This is what the memory will look like after we store:
value 7 in address 1, value 3 in address 2, value 8 in address 5, and value 255 in address 6.

Address	Content	
0	00000000	(8 bits)
1	00000111	(8 bits)
2	00000011	(8 bits)
3	00000000	(8 bits)
4	00000000	(8 bits)
5	00001000	(8 bits)
6	11111111	(8 bits)
7	00000000	(8 bits)

How to store characters in memory

- Since the computer machine can only understand binary numbers, the character set is represented by number.
- Example: Upper case character A is represented by the number 65 in base 10 which is 01000001 in binary.
- The ASCII character code tables contain the decimal values of the extended ASCII (American Standards Committee for Information Interchange) character set.
- The extended character set includes the ASCII character set and 128 other characters for graphics and line drawing, often called the “IBM ® character set.”


IBM All Character 437 Set (ANSI)

	00	01	02	03	04	05	06	07	08	09	0A	0B	0C	0D	0E	0F
	<u>0</u>	<u>1</u>	<u>2</u>	<u>3</u>	<u>4</u>	<u>5</u>	<u>6</u>	<u>7</u>	<u>8</u>	<u>9</u>	<u>10</u>	<u>11</u>	<u>12</u>	<u>13</u>	<u>14</u>	<u>15</u>
00	<u>0</u>		☺	☻	♥	♦	♣	♠	•	◼	◻	♂	♀		♪	✳
10	<u>16</u>	▶	◀	↕	!!	¶	§	—	↕	↑	↓	→	←	↲	↻	▼
20	<u>32</u>		!	"	#	\$	%	&	'	()	*	+	,	-	/
30	<u>48</u>	Ø	1	2	3	4	5	6	7	8	9	:	;	<	=	> ?
40	<u>64</u>	@	A	B	C	D	E	F	G	H	I	J	K	L	M	N O
50	<u>80</u>	P	Q	R	S	T	U	V	W	X	Y	Z	[\]	^ _
60	<u>96</u>	'	a	b	c	d	e	f	g	h	i	j	k	l	m	n o
70	<u>112</u>	p	q	r	s	t	u	v	w	x	y	z	{		}	~ Δ
80	<u>128</u>	Ç	ü	é	â	ä	à	å	ç	ê	ë	è	ï	î	ì	Ä Å
90	<u>144</u>	É	æ	Æ	ô	ö	ò	û	ù	y	ÿ	Ü	φ	£	¥	℞ f
A0	<u>160</u>	á	í	ó	ú	ñ	Ñ	ä	ö	¿	¬	¬	½	¼	♠	«»
B0	<u>176</u>	▒	▒	▒		+	+	+	+	+	+	+	+	+	+	+
C0	<u>192</u>	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂
D0	<u>208</u>	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂	⌂
E0	<u>224</u>	α	β	Γ	π	Σ	σ	μ	τ	ϑ	θ	Ω	δ	∞	∅	ε η
F0	<u>240</u>	≡	±	≥	≤	∫	∫	÷	≈	°	•	•	√	η	z	■

How to store characters in memory. Example

- If we want to write the word “Hello!” in a memory of size 8 bytes.

Address	Content base 2	Content base 10
0	00110000	48
1	01100101	101
2	01101100	108
3	01101100	108
4	01101111	111
5	00100001	33
6	00000000	00
7	00000000	00

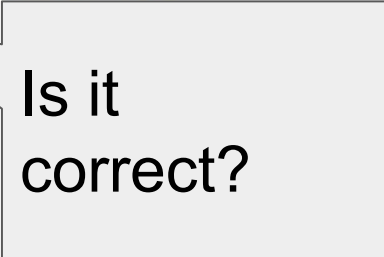

Is it correct?

Big- and Little-Endian Formats

- Computers are designed around two different architectures based on the order in which bytes are stored in memory:
 - **Big-Endian** (from 'Big End In') and
 - **Little-Endian**.
- On an Intel based CPU computer, the little-end (least significant byte) is stored first.
- On a Motorola based CPU computer, the big-end (most significant byte) is stored first.

Big- and Little-Endian Formats

- IEEE 754 floating-point standard does not specify endianness
- We will assume that the endianness is the same for floating-point numbers as for integers

Big- and Little-Endian Formats

- Little-Endian Example:
 - A 4-byte value like 0x87654321 would be stored as 0x21 0x43 0x65 0x87.
- Big-Endian Example:
 - A 4-byte value like 0x87654321 would be stored as 0x87 0x65 0x43 0x21.

Big- and Little-Endian Formats

- Let's see what the Little-Endian based memory will look like after we store value $258_{10} = 00000001\ 00000010_2 = 0102_{16}$ in address 4.

Address	Content base 2	Content base 16	
0	00000000	00	(8 bits)
1	00000000	00	(8 bits)
2	00000000	00	(8 bits)
3	00000000	00	(8 bits)
4	00000010	02	(8 bits)
5	00000001	01	(8 bits)
6	00000000	00	(8 bits)
7	00000000	00	(8 bits)

Big- and Little-Endian Conversion

```
/* C function to change endianness for byte  
swap in an unsigned 32-bit integer */
```

```
uint32_t ChangeEndianness(uint32_t value)  
{  
    uint32_t result = 0;  
    result |= (value & 0x000000FF) << 24;  
    result |= (value & 0x0000FF00) << 8;  
    result |= (value & 0x00FF0000) >> 8;  
    result |= (value & 0xFF000000) >> 24;  
    return result;  
}
```

Big- and Little-Endian Determination

```
int is_big_endian(void)
{
    union {
        uint32_t i;
        char c[4];
    } e = { 0x01000000 };

    return e.c[0];
}
```

Self-test question

The unsigned integer 3,505,468,161 can be written in 32-bit binary as 11010000 11110001 00110011 00000001. Putting it into four bytes of memory beginning at address 98370 in little endian fashion would give which picture?

- ☐

98370	98371	98372	98373
11010000	11110001	00110011	00000001
- ☐

98370	98371	98372	98373
00000001	11110001	00110011	11010000
- ☐

98370	98371	98372	98373
00000001	00110011	11110001	11010000
- ☐

98370	98371	98372	98373
00110011	00000001	11010000	11110001

Self-test question

Why is it necessary to know whether a computer is big-endian or little-endian?

- A) because some programs write integers to memory in a certain order
- B) because arithmetic errors can result if the computer gets the numbers backward
- C) because sharing files and data between different computers can result in misinterpretation

References

- https://en.wikipedia.org/wiki/Address_decoder
- <https://en.wikipedia.org/wiki/ASCII>
- <https://en.wikipedia.org/wiki/Endianness>